

# PHYSICS 1003/1902

## Mid-Semester Test SAMPLE: SOLUTIONS

<b>Surname</b>				<b>First name</b>			
<b>SID</b>				<b>Team no. (e.g. 6TEC12)</b>			
<b>Q1 /4</b>	<b>Q2 /4</b>	<b>Q3 /4</b>	<b>Q4 /4</b>	<b>Q5 /4</b>	<b>Q6 /10</b>	<b>Q7 /10</b>	<b>Total mark /40</b>

Duration **60** minutes + 5 minutes reading time. CLOSED BOOK test.

Questions 1–5 are worth 4 marks each; questions 6 and 7 are worth 10 marks each.

There should be sufficient space for working, but only the final answer is checked.

**All numerical answers must have appropriate units and significant figures**

### DATA

Permittivity of free space	$\varepsilon_0 = 8.854 \times 10^{-12} \text{ F.m}^{-1}$
Permeability of free space	$\mu_0 = 4\pi \times 10^{-7} \text{ T.m.A}^{-1}$
Elementary charge	$e = 1.602 \times 10^{-19} \text{ C}$
Local gravitational acceleration	$g = 9.80 \text{ m.s}^{-2}$

### FORMULAS

$$F = ma$$

$$V = IR$$

$$V_{ab} = E d$$

$$\varepsilon = vBL$$

$$R_{\text{total}} = R_1 + R_2$$

$$v_{\text{out}} = \frac{v_{\text{in}} R_2}{R_1 + R_2}$$

$$v = V_0 e^{j\omega t} = V_0 \cos(\omega t) + jV_0 \sin(\omega t)$$

$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{f_0}{f_2 - f_1} = R \sqrt{\frac{C}{L}}$$

$$v_{\text{out}} = \frac{v_{\text{in}} Z_2}{Z_1 + Z_2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$E = \frac{\sigma}{\varepsilon_0} = \frac{Q}{\varepsilon_0 A}$$

$$\vec{F} = i \vec{l} \times \vec{B}$$

$$C = \frac{Q}{V_{ab}} = \varepsilon_0 \frac{A}{d} \quad (\text{parallel plates})$$

$$F_B = ILB$$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$Z = R + jX$$


$$X_C = -\frac{1}{\omega C}$$

$$X_L = \omega L$$

$$Z_{\text{total}} = Z_1 + Z_2$$

$$\frac{1}{Z_{\text{total}}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\omega = 2\pi f$$

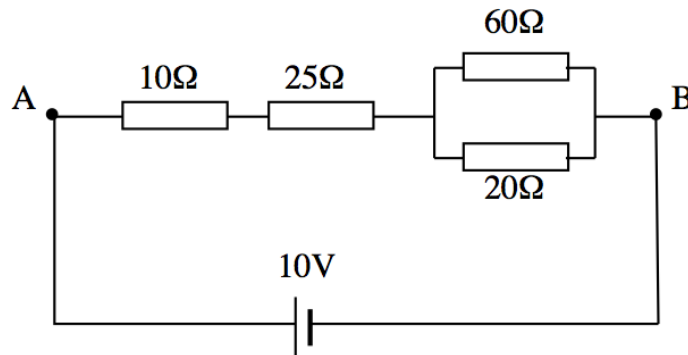
**Question 1****[Total: 4 marks]**

- (a) What is the resistance between the terminals A and B?

**50 Ω****(2 marks)**

- (b) Calculate the current through the 60 Ω resistor.

**0.05 A****(2 marks)**

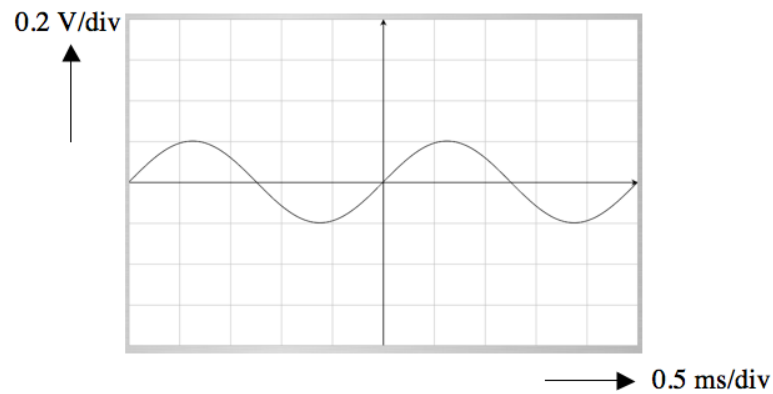**Question 2****[Total: 4 marks]**

The above signal is observed on an oscilloscope with its controls set as indicated.

- (a) What is the amplitude of the signal?

**0.2 V**

**(2 marks)**


- (b) What is the frequency of the signal?

**400 Hz**

**(2 marks)**

## Question 3

[Total: 4 marks]

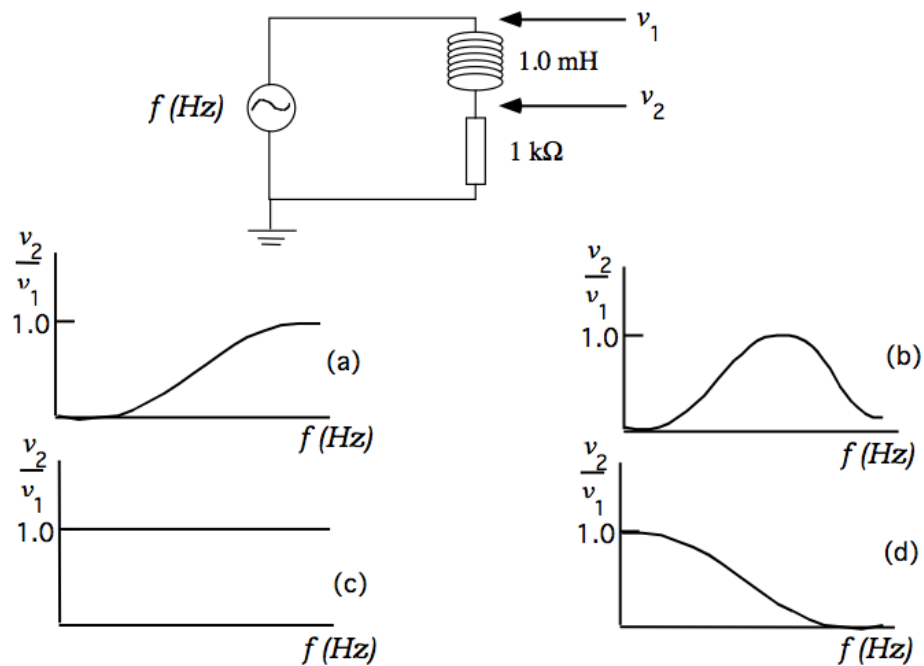

- (a) Which of the graphs (a) to (d) best represents the ratio  $v_2/v_1$  vs  $f$  in this circuit?

(d)

(2 marks)


- (b) What is this circuit used for?

**Low-pass filter: low frequencies are passed unchanged, but high frequencies are attenuated.**

(2 marks)

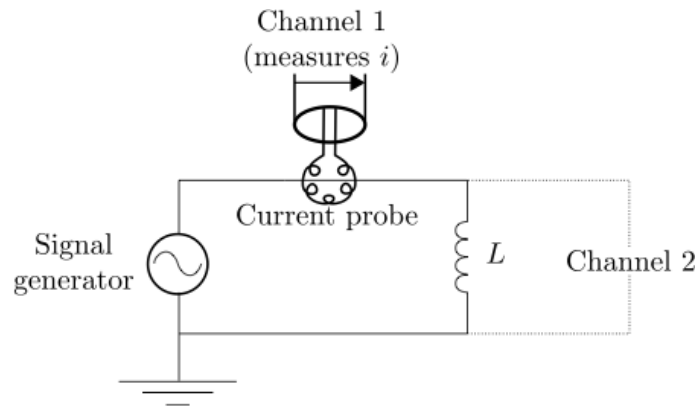**Question 4****[Total: 4 marks]**

The signal generator in the circuit shown below has a sine wave output of amplitude 10 V (measured by channel 2 of an oscilloscope), at a frequency of 15 kHz. The inductor has  $L = 10 \text{ mH}$ .



- (a) Calculate the amplitude of the current measured by the current probe (Channel 1).


**11 mA****(2 marks)**

- (b) Does the current lead or lag the voltage across the inductor?


**Lags****(2 marks)**

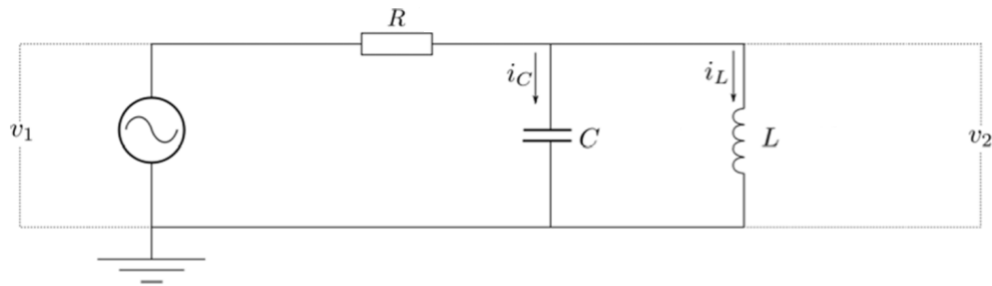**Question 5****[Total: 4 marks]**

In the RLC circuit below,  $R = 10.0 \text{ k}\Omega$ ,  $C = 10.0 \text{ nF}$ , and  $L = 10.0 \text{ mH}$ ,



- (a) Sketch the frequency response of the above circuit.

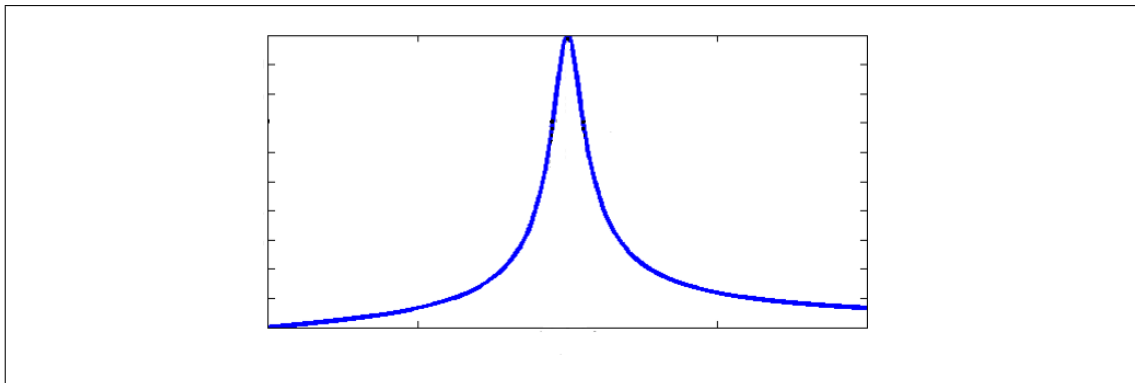**(2 marks)**

- (b) Calculate the quality factor of the circuit.

**10****(2 marks)**

**Question 6****[Total: 10 marks]**

A horizontal parallel plate capacitor with plates of area  $A = 1 \text{ m}^2$  separated by distance  $d = 0.02 \text{ m}$  has a charge  $Q = 4 \times 10^{-10} \text{ C}$  on the upper plate and  $-Q$  on the lower one.

- (a) Find the strength and direction of the electric field between the plates.

**45 N/C, down**

**(2 marks)**

- (b) What is the capacitance of the capacitor?

**$4.4 \times 10^{-10} \text{ F}$**

**(2 marks)**

- (c) What is the magnitude and direction of the electric force acting on an electron between the plates of the capacitor?

**$7.2 \times 10^{-18} \text{ N, up}$**

**(2 marks)**

- (d) Compare the electric force with the gravitational force acting on the electron. Which way will the electron go?

**$F_W = 9 \times 10^{-30} \text{ N} \ll F_E; \text{ up}$**

**(2 marks)**


- (e) If an electron is placed in the middle of the capacitor, how long would it take for it to hit one of the plates?

**$t = 5 \times 10^{-8} \text{ s}$**

**(2 marks)**

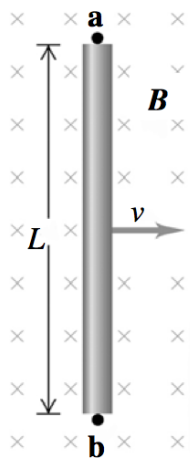**Question 7****[Total: 10 marks]**

A conducting rod with length  $L = 0.500$  m moves in a magnetic field  $B$  of magnitude  $0.600$  T directed into the plane of the figure below. The rod moves with velocity  $v = 4.50$  m.s<sup>-1</sup> in the direction shown.



- (a) Calculate the motional emf induced in the rod.

1.35 V

(3 marks)

- (b) What is the potential difference between the ends of the rod?

1.35 V

(2 marks)

- (c) Which point, a or b, is at higher potential?

a

(2 marks)

- (d) When the charges in the rod are in equilibrium, what is the magnitude and direction of the electric field within the rod?

2.7 V.m<sup>-1</sup>, a → b

(3 marks)

**THERE ARE NO MORE QUESTIONS.**