PHYSICS 1003/1902 Mid-Semester Test SAMPLE

Surname				First name								
SID				Team no. (e.g. 6TEC12)								
Q1 /4	Q2 /4	Q3 /4	Q4	/4	Q5	/4	Q6	/10	Q7	/10	Total mark	/40

Duration 60 minutes + 5 minutes reading time. CLOSED BOOK test.

Questions 1–5 are worth 4 marks each; questions 6 and 7 are worth 10 marks each.

There should be sufficient space for working, but only the final answer is checked.

All numerical answers must have appropriate units and significant figures

DATA

Permittivity of free space $\varepsilon_0 = 8.854 \times 10^{-12} \; \mathrm{F.m^{-1}}$ Permeability of free space $\mu_0 = 4\pi \times 10^{-7} \; \mathrm{T.m.A^{-1}}$ Elementary charge $e = 1.602 \times 10^{-19} \; \mathrm{C}$ Local gravitational acceleration $q = 9.80 \; \mathrm{m.s^{-2}}$

FORMULAS

$$F = ma$$

$$V = IR$$

$$V_{ab} = E d$$

$$\varepsilon = vBL$$

$$R_{total} = R_1 + R_2$$

$$v_{out} = \frac{v_{in}R_2}{R_1 + R_2}$$

$$v = V_0e^{j\omega t} = V_0\cos(\omega t) + jV_0\sin(\omega t)$$

$$Q = \frac{f_0}{f_2 - f_1} = R\sqrt{\frac{C}{L}}$$

$$v_{out} = \frac{v_{in}Z_2}{Z_1 + Z_2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$E = \frac{\sigma}{\varepsilon_0} = \frac{Q}{\varepsilon_0 A}$$

$$C = \frac{Q}{V_{ab}} = \varepsilon_0 \frac{A}{d} \text{ (parallel plates)}$$

$$F_B = ILB$$

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$Z = R + jX$$

$$X_C = -\frac{1}{\omega C}$$


$$X_L = \omega L$$

$$Z_{total} = Z_1 + Z_2$$


$$\frac{1}{Z_{total}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\omega = 2\pi f$$


Question 1 [Total: 4 marks]

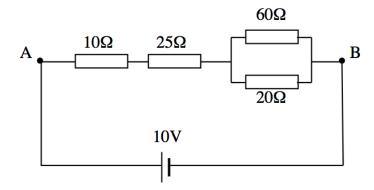

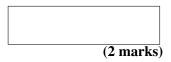(a) What is the resistance between the terminals A and B?




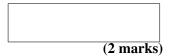
(b) Calculate the current through the $60~\Omega$ resistor.



_


Question 2

 

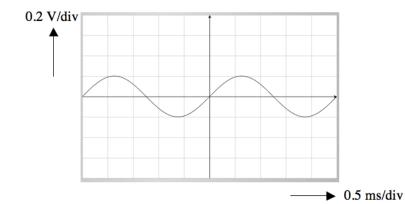


The above signal is observed on an oscilloscope with its controls set as indicated.


(a) What is the amplitude of the signal?

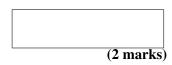

(b) What is the frequency of the signal?

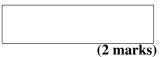

Question 3 [Total: 4 marks]

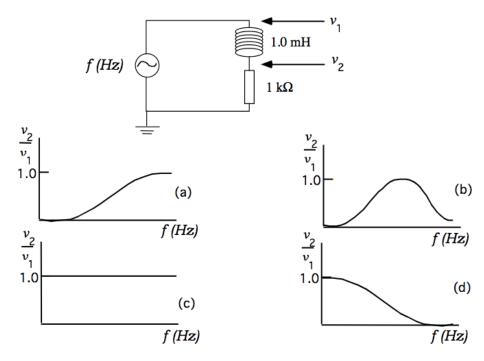

(a) Which of the graphs (a) to (d) best represents the ratio v_2/v_1 vs f in this circuit?


(2 marks

(b) What is this circuit used for?


(2 marks)

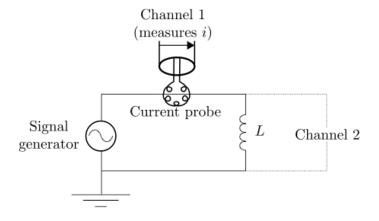Question 4 [Total: 4 marks]

The signal generator in the circuit shown below has a sine wave output of amplitude 10 V (measured by channel 2 of an oscilloscope), at a frequency of 15 kHz. The inductor has $L=10~\mathrm{mH}$.



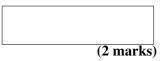(a) Calculate the amplitude of the current measured by the current probe (Channel 1).




(b) Does the current lead or lag the voltage across the inductor?



(2 marks)

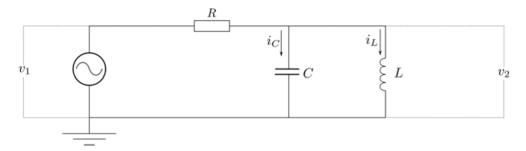Question 5 [Total: 4 marks]

In the RLC circuit below, $R=10.0~\mathrm{k}\Omega,\,C=10.0~\mathrm{nF},$ and $L=10.0~\mathrm{mH},$




(a) Sketch the frequency response of the above circuit.



(2 marks)

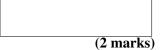(b) Calculate the quality factor of the circuit.




Question 6	[Total:	10 m	arks	;]
------------	---------	------	------	----

A horizontal parallel plate capacitor with plates of area $A=1~\mathrm{m^2}$ separated by distance $d=0.02~\mathrm{m}$ has a charge $Q=4\times10^{-10}~\mathrm{C}$ on the upper plate and -Q on the lower one.

(a)	Find the strength and direction of the electric field between the plates.
	(2 marks
(b)	What is the capacitance of the capacitor?
	(2 marks
(c)	What is the magnitude and direction of the electric force acting on an electron between the plates of the capacitor?
	(2 marks
(d)	Compare the electric force with the gravitational force acting on the electron. Which way will the electron go?
	(2 marks
(e)	If an electron is placed in the middle of the capacitor, how long would it take for it to hit one of the plates?
	(2 marks

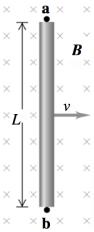Question 7 [Total: 10 marks]

A conducting rod with length $L=0.500~\mathrm{m}$ moves in a magnetic field B of magnitude $0.600~\mathrm{T}$ directed into the plane of the figure below. The rod moves with velocity $v=4.50~\mathrm{m.s^{-1}}$ in the direction shown.



(a)	Calculate the motional emf induced in the rod.	
		(3 marks)
(b)	What is the potential difference between the ends of the rod?	
		(2 marks)
(c)	Which point, a or b, is at higher potential?	
		(2 marks)
(d)	When the charges in the rod are in equilibrium, what is the magnitude	de and direction of the electric

(3 marks)

field within the rod?

THERE ARE NO MORE QUESTIONS.